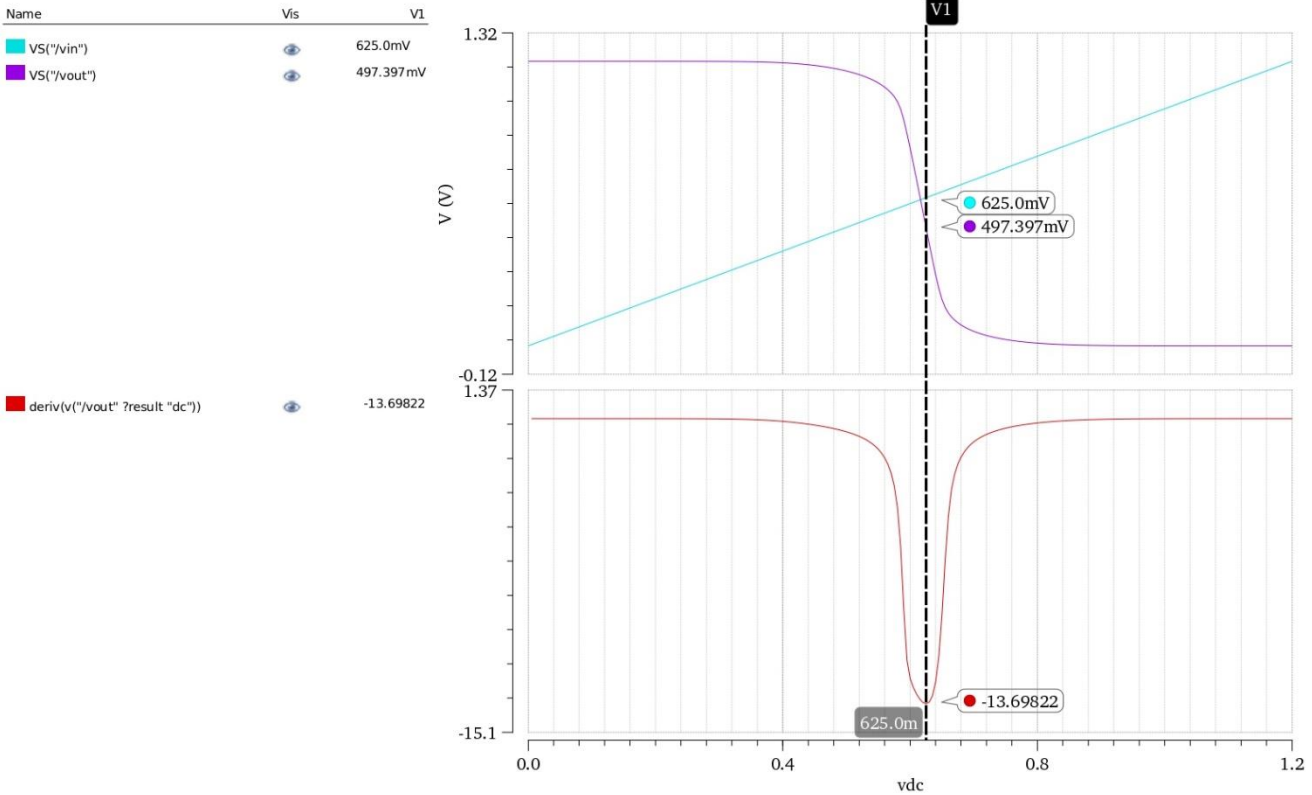


DC voltage sweep:

DC Analysis `dc': vdc = (0 -> 1.2)




Markers


## AC Gain vs freq:

tutorial\_inverter\_1 : tutorial inverter schematic

21:15:23 Mon Sep 9 2024

### AC Response

Name	Vis
<span style="color: green;">■</span> mag(VF("/vout"))	

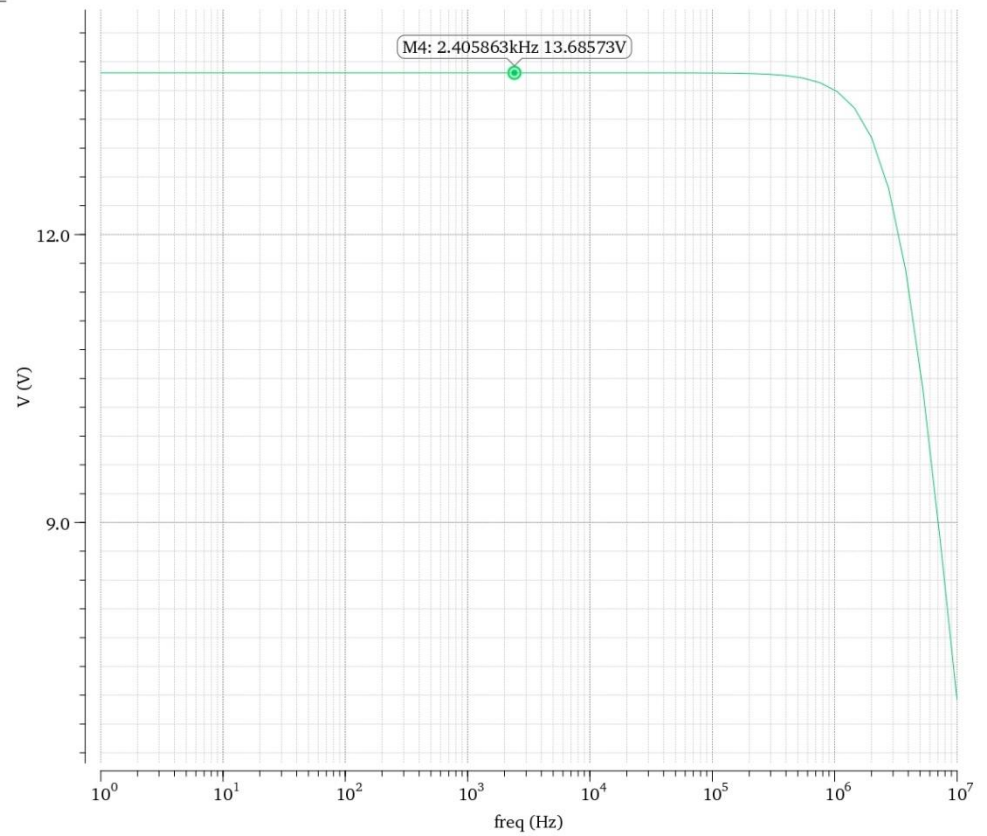

# Transient signals:

