
Layout Screenshot:

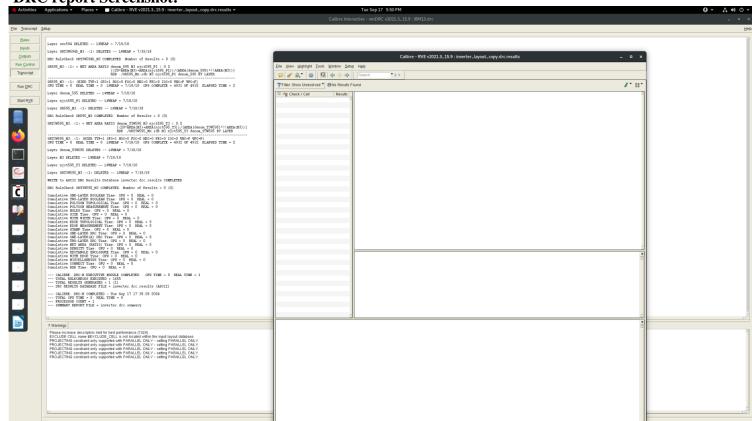


DRC report Screenshot:




LVS report Screenshot:

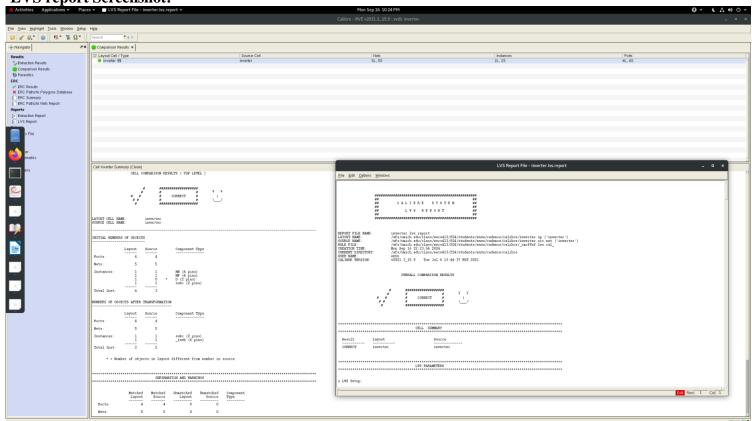Applications - Places - LVS Report File - Invertex Just report




AC Gain magnitude for Schematic and PEX view:

test dc:

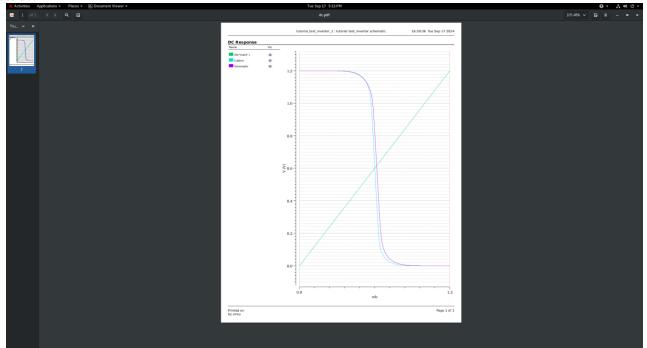



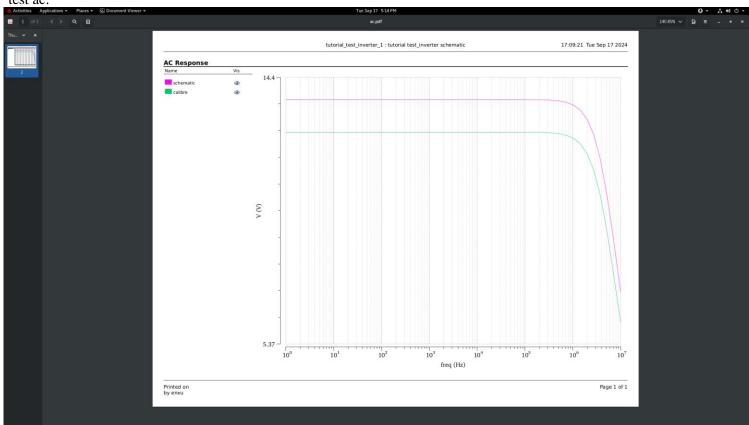

The calibre generally has a lower magnitude than the schematic. This is because with the parasitic capacitors simulated, the low frequency signals are more attenuated.